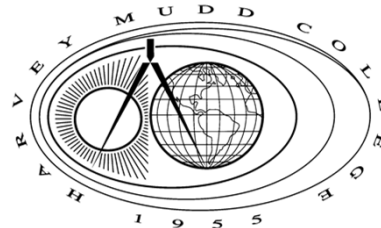


Introduction to CMOS VLSI Design

Lecture 12: Datapath Functional Units

David Harris



Harvey Mudd College

Spring 2004

Outline




- Comparators
- Shifters
- Multi-input Adders
- Multipliers

Comparators

- ❑ 0's detector: $A = 00\dots000$
- ❑ 1's detector: $A = 11\dots111$
- ❑ Equality comparator: $A = B$
- ❑ Magnitude comparator: $A < B$


1's & 0's Detectors

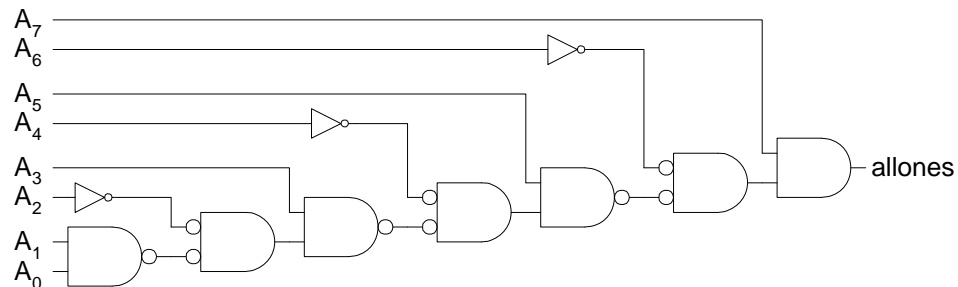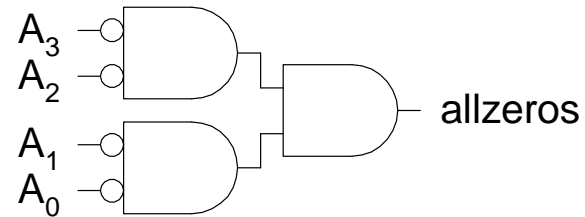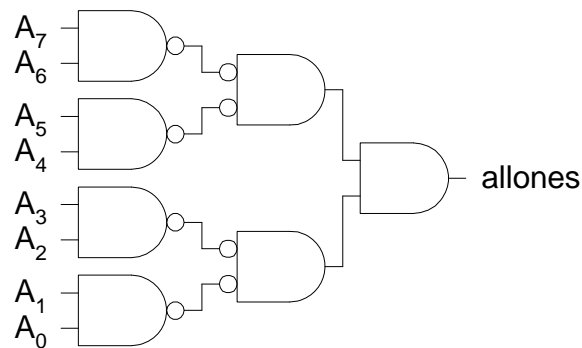- ❑ 1's detector: N-input AND gate
- ❑ 0's detector: NOTs + 1's detector (N-input NOR)




Equality Comparator

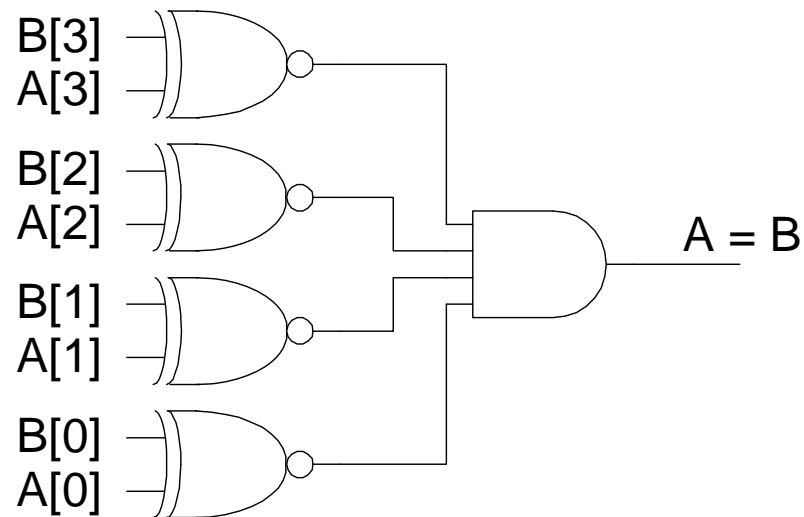- ❑ Check if each bit is equal (XNOR, aka equality gate)
- ❑ 1's detect on bitwise equality



Magnitude Comparator

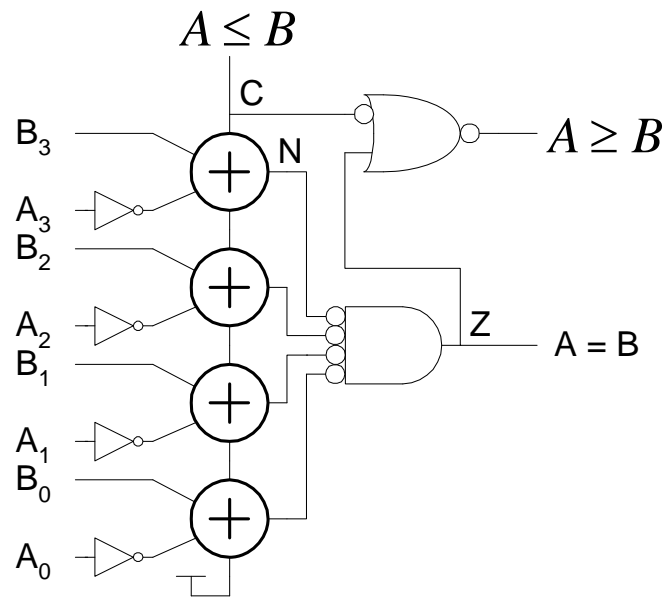- ❑ Compute $B-A$ and look at sign
- ❑ $B-A = B + \sim A + 1$
- ❑ For unsigned numbers, carry out is sign bit



Signed vs. Unsigned

- For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of A-B are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign \neq B)

Table 10.4 Magnitude comparison

| Relation | Unsigned Comparison | Signed Comparison |
|------------|---------------------|-------------------------------|
| $A = B$ | Z | Z |
| $A \neq B$ | \bar{Z} | \bar{Z} |
| $A < B$ | $\overline{C + Z}$ | $\overline{(N \oplus V) + Z}$ |
| $A > B$ | \bar{C} | $(N \oplus V)$ |
| $A \leq B$ | C | $\overline{(N \oplus V)}$ |
| $A \geq B$ | $\bar{C} + Z$ | $(N \oplus V) + Z$ |

Shifters

□ Logical Shift:

– Shifts number left or right and fills with 0's

• 1011 LSR 1 = _____ 1011 LSL1 = _____

□ Arithmetic Shift:

– Shifts number left or right. Rt shift sign extends

• 1011 ASR1 = _____ 1011 ASL1 = _____

□ Rotate:

– Shifts number left or right and fills with lost bits

• 1011 ROR1 = _____ 1011 ROL1 = _____

Shifters

□ Logical Shift:

– Shifts number left or right and fills with 0's

- $1011 \text{ LSR } 1 = 0101$ $1011 \text{ LSL } 1 = 0110$

□ Arithmetic Shift:

– Shifts number left or right. Rt shift sign extends

- $1011 \text{ ASR } 1 = 1101$ $1011 \text{ ASL } 1 = 0110$


□ Rotate:

– Shifts number left or right and fills with lost bits

- $1011 \text{ ROR } 1 = 1101$ $1011 \text{ ROL } 1 = 0111$

Funnel Shifter

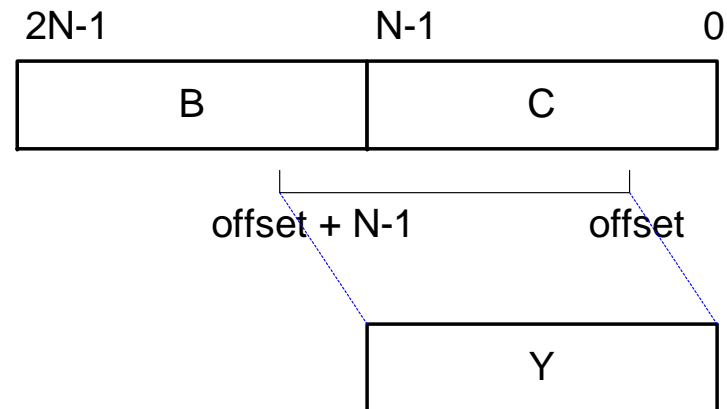- ❑ A funnel shifter can do all six types of shifts
- ❑ Selects N-bit field Y from 2N-bit input
 - Shift by k bits ($0 \leq k < N$)



Funnel Shifter Operation

Table 10.10 Funnel shifter operation

| Shift Type | B | C | Offset |
|------------------|--------------------|--------------------|--------|
| Logical Right | $0\dots 0$ | $A_{N-1}\dots A_0$ | k |
| Logical Left | $A_{N-1}\dots A_0$ | $0\dots 0$ | $N-k$ |
| Arithmetic Right | | | |
| Arithmetic Left | | | |
| Rotate Right | | | |
| Rotate Left | | | |

- ❑ Computing $N-k$ requires an adder

Funnel Shifter Operation

Table 10.10 Funnel shifter operation

| Shift Type | B | C | Offset |
|------------------|--|--------------------|--------|
| Logical Right | $0\dots 0$ | $A_{N-1}\dots A_0$ | k |
| Logical Left | $A_{N-1}\dots A_0$ | $0\dots 0$ | $N-k$ |
| Arithmetic Right | $A_{N-1}\dots A_{N-1}$ (sign extension) | $A_{N-1}\dots A_0$ | k |
| Arithmetic Left | | | |
| Rotate Right | | | |
| Rotate Left | | | |

- ❑ Computing $N-k$ requires an adder

Funnel Shifter Operation

Table 10.10 Funnel shifter operation

| Shift Type | B | C | Offset |
|------------------|--|--------------------|--------|
| Logical Right | $0\dots 0$ | $A_{N-1}\dots A_0$ | k |
| Logical Left | $A_{N-1}\dots A_0$ | $0\dots 0$ | $N-k$ |
| Arithmetic Right | $A_{N-1}\dots A_{N-1}$ (sign extension) | $A_{N-1}\dots A_0$ | k |
| Arithmetic Left | $A_{N-1}\dots A_0$ | 0 | $N-k$ |
| Rotate Right | | | |
| Rotate Left | | | |

- ❑ Computing $N-k$ requires an adder

Funnel Shifter Operation

Table 10.10 Funnel shifter operation

| Shift Type | B | C | Offset |
|------------------|--|--------------------|--------|
| Logical Right | $0\dots 0$ | $A_{N-1}\dots A_0$ | k |
| Logical Left | $A_{N-1}\dots A_0$ | $0\dots 0$ | $N-k$ |
| Arithmetic Right | $A_{N-1}\dots A_{N-1}$ (sign extension) | $A_{N-1}\dots A_0$ | k |
| Arithmetic Left | $A_{N-1}\dots A_0$ | 0 | $N-k$ |
| Rotate Right | $A_{N-1}\dots A_0$ | $A_{N-1}\dots A_0$ | k |
| Rotate Left | | | |

- ❑ Computing $N-k$ requires an adder

Funnel Shifter Operation

Table 10.10 Funnel shifter operation

| Shift Type | B | C | Offset |
|------------------|--|--------------------|--------|
| Logical Right | $0\dots 0$ | $A_{N-1}\dots A_0$ | k |
| Logical Left | $A_{N-1}\dots A_0$ | $0\dots 0$ | $N-k$ |
| Arithmetic Right | $A_{N-1}\dots A_{N-1}$ (sign extension) | $A_{N-1}\dots A_0$ | k |
| Arithmetic Left | $A_{N-1}\dots A_0$ | 0 | $N-k$ |
| Rotate Right | $A_{N-1}\dots A_0$ | $A_{N-1}\dots A_0$ | k |
| Rotate Left | $A_{N-1}\dots A_0$ | $A_{N-1}\dots A_0$ | $N-k$ |

- ❑ Computing $N-k$ requires an adder

Simplified Funnel Shifter

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

| Shift Type | Z | Offset |
|------------------|-----------------------|-----------|
| Logical Right | $0..0, A_{N-1}...A_0$ | k |
| Logical Left | $A_{N-1}...A_0, 0..0$ | \bar{k} |
| Arithmetic Right | | |
| Arithmetic Left | | |
| Rotate Right | | |
| Rotate Left | | |

Simplified Funnel Shifter

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

| Shift Type | Z | Offset |
|------------------|------------------------------------|-----------|
| Logical Right | $0..0, A_{N-1}...A_0$ | k |
| Logical Left | $A_{N-1}...A_0, 0..0$ | \bar{k} |
| Arithmetic Right | $A_{N-1}...A_{N-1}, A_{N-1}...A_0$ | k |
| Arithmetic Left | | |
| Rotate Right | | |
| Rotate Left | | |

Simplified Funnel Shifter

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

| Shift Type | Z | Offset |
|------------------|------------------------------------|-----------|
| Logical Right | $0..0, A_{N-1}...A_0$ | k |
| Logical Left | $A_{N-1}...A_0, 0..0$ | \bar{k} |
| Arithmetic Right | $A_{N-1}...A_{N-1}, A_{N-1}...A_0$ | k |
| Arithmetic Left | $A_{N-1}...A_0, 0..0$ | \bar{k} |
| Rotate Right | | |
| Rotate Left | | |

Simplified Funnel Shifter

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

| Shift Type | Z | Offset |
|------------------|------------------------------------|-----------|
| Logical Right | $0..0, A_{N-1}...A_0$ | k |
| Logical Left | $A_{N-1}...A_0, 0..0$ | \bar{k} |
| Arithmetic Right | $A_{N-1}...A_{N-1}, A_{N-1}...A_0$ | k |
| Arithmetic Left | $A_{N-1}...A_0, 0..0$ | \bar{k} |
| Rotate Right | $A_{N-2}...A_0, A_{N-1}...A_0$ | k |
| Rotate Left | | |

Simplified Funnel Shifter


- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

| Shift Type | Z | Offset |
|------------------|----------------------------------|-----------|
| Logical Right | $0..0, A_{N-1}..A_0$ | k |
| Logical Left | $A_{N-1}..A_0, 0..0$ | \bar{k} |
| Arithmetic Right | $A_{N-1}..A_{N-1}, A_{N-1}..A_0$ | k |
| Arithmetic Left | $A_{N-1}..A_0, 0..0$ | \bar{k} |
| Rotate Right | $A_{N-2}..A_0, A_{N-1}..A_0$ | k |
| Rotate Left | $A_{N-1}..A_0, A_{N-1}..A_1$ | \bar{k} |


Funnel Shifter Design 1

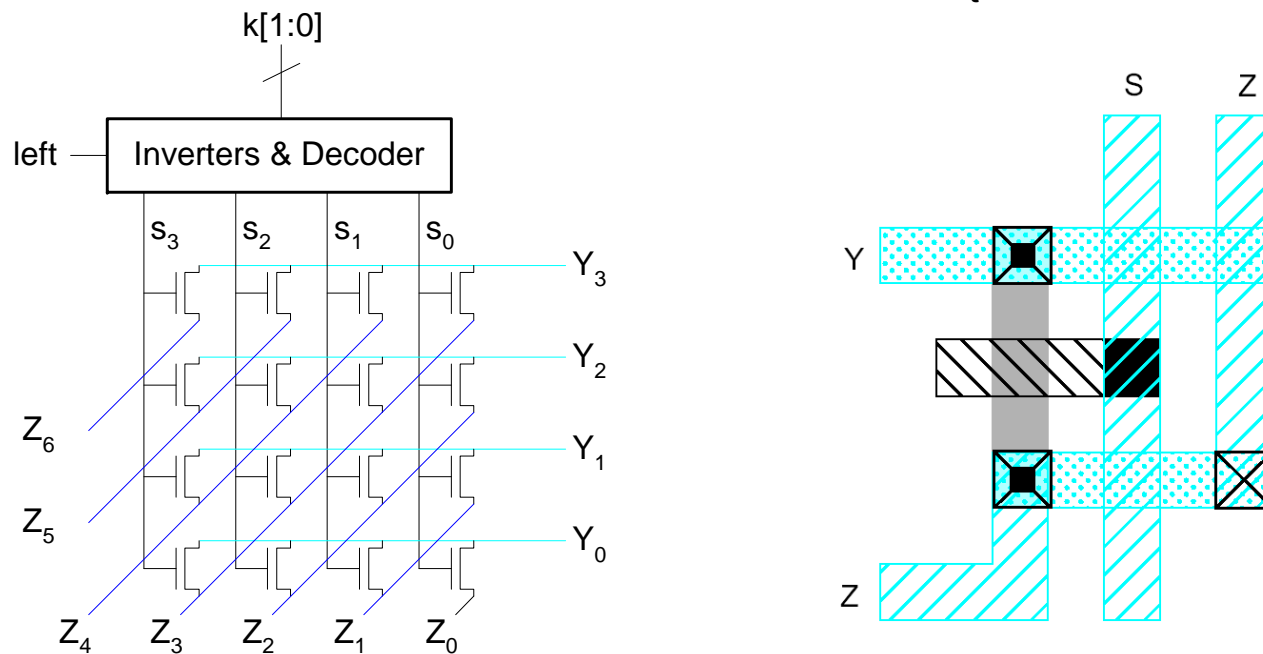- N N-input multiplexers
 - Use 1-of-N hot select signals for shift amount
 - nMOS pass transistor design (V_t drops!)



Funnel Shifter Design 2

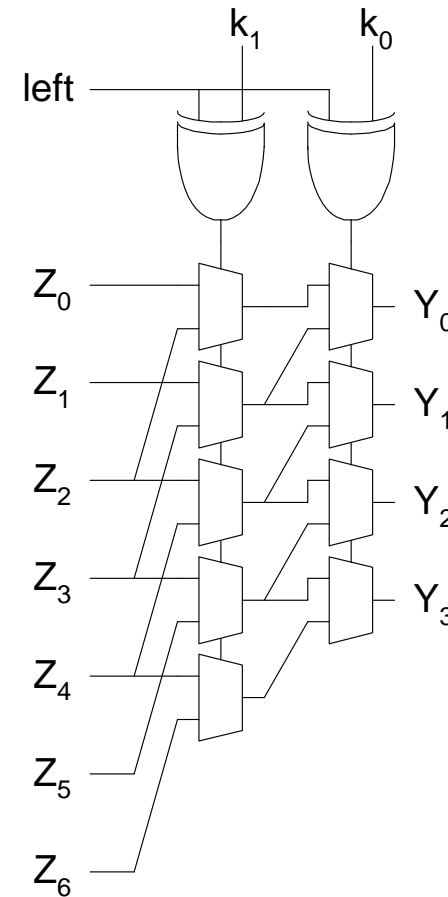- Log N stages of 2-input muxes
 - No select decoding needed



Multi-input Adders

- Suppose we want to add k N-bit words


– Ex: $0001 + 0111 + 1101 + 0010 = \underline{\hspace{2cm}}$

Multi-input Adders

- Suppose we want to add k N-bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = 10111$


Multi-input Adders

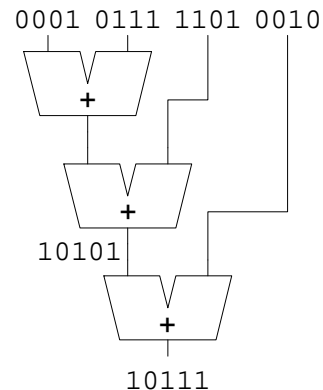- ❑ Suppose we want to add k N -bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = 10111$
- ❑ Straightforward solution: $k-1$ N -input CPAs
 - Large and slow




Carry Save Addition

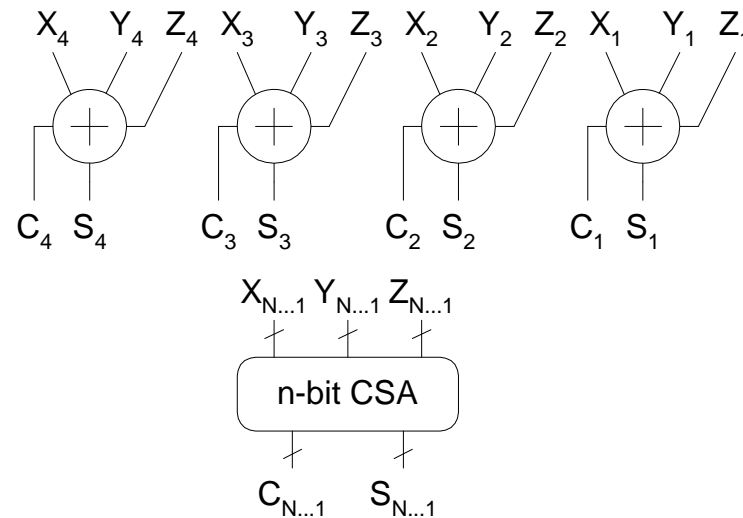- ❑ A full adder sums 3 inputs and produces 2 outputs
 - Carry output has twice *weight* of sum output
- ❑ N full adders in parallel are called *carry save adder*
 - Produce N sums and N carry outs




CSA Application

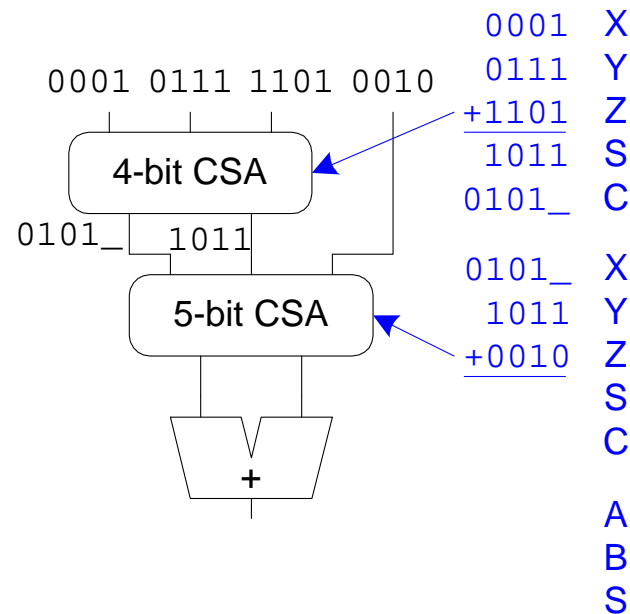- ❑ Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- ❑ Final CPA computes actual result




CSA Application

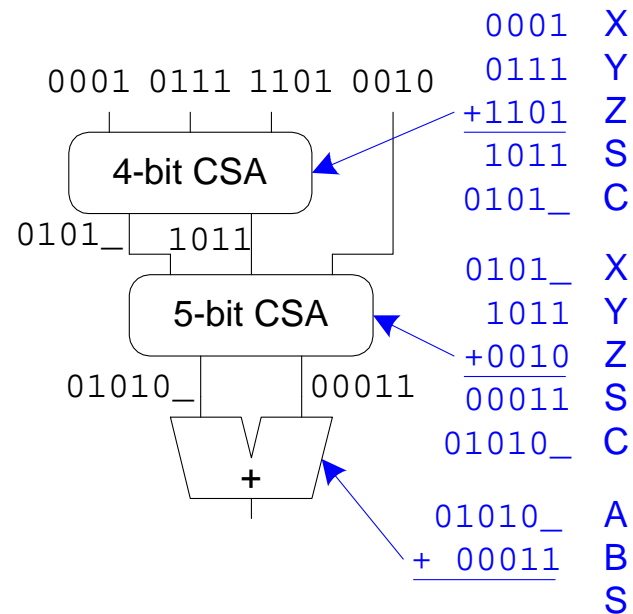- ❑ Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- ❑ Final CPA computes actual result



CSA Application

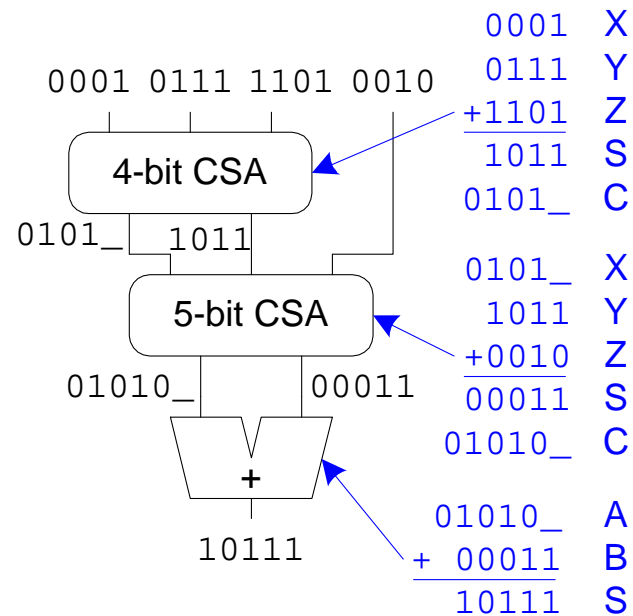- ❑ Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- ❑ Final CPA computes actual result



Multiplication

□ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ \underline{0101} : 5_{10} \end{array}$$

Multiplication

□ Example:

$$\begin{array}{r} 1100 \\ \times 0101 \\ \hline 1100 \\ 1100 \\ \hline 1100 \end{array}$$

Multiplication

□ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ \hline \end{array}$$

Multiplication

□ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ \hline \end{array}$$

Multiplication

□ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline \end{array}$$

Multiplication

□ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 00111100 : 60_{10} \end{array}$$

Multiplication

□ Example:

$$\begin{array}{r} 1100 \\ \times 0101 \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 00111100 \end{array}$$

12_{10}

5_{10}

multiplicand

multiplier

partial
products


product

□ M x N-bit multiplication


- Produce N M-bit partial products
- Sum these to produce M+N-bit product

Dot Diagram

- Each dot represents a bit

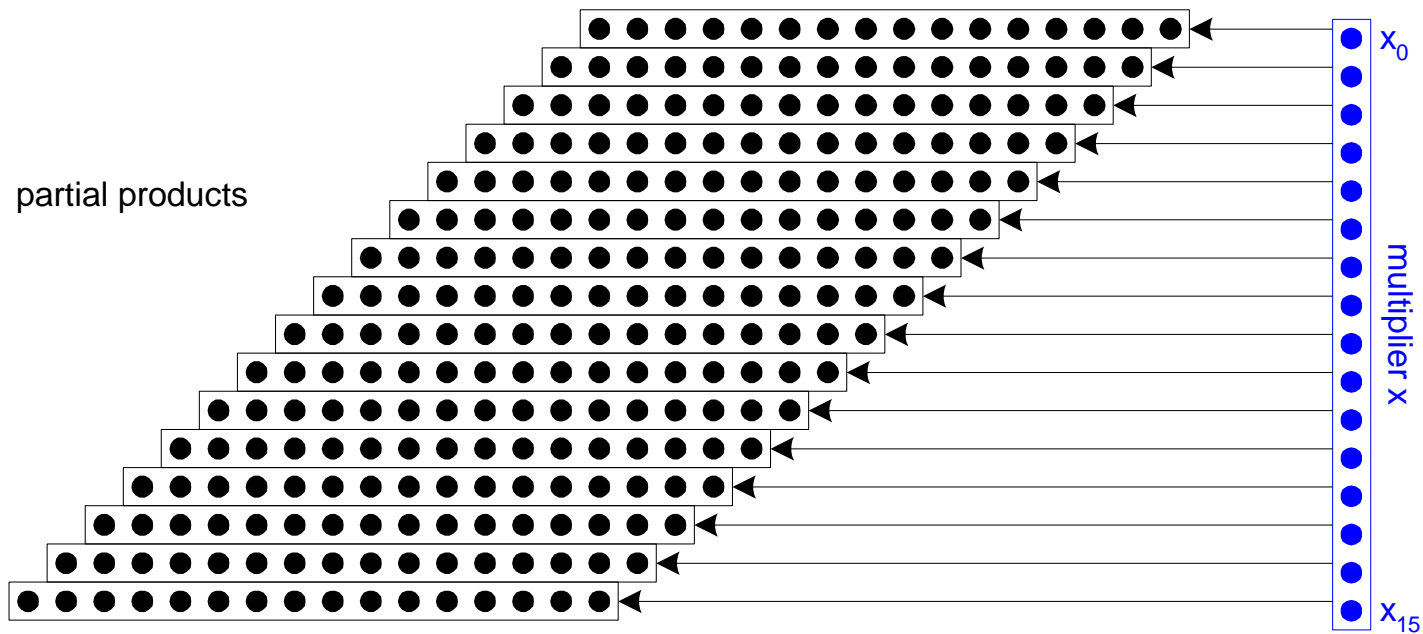


Array Multiplier

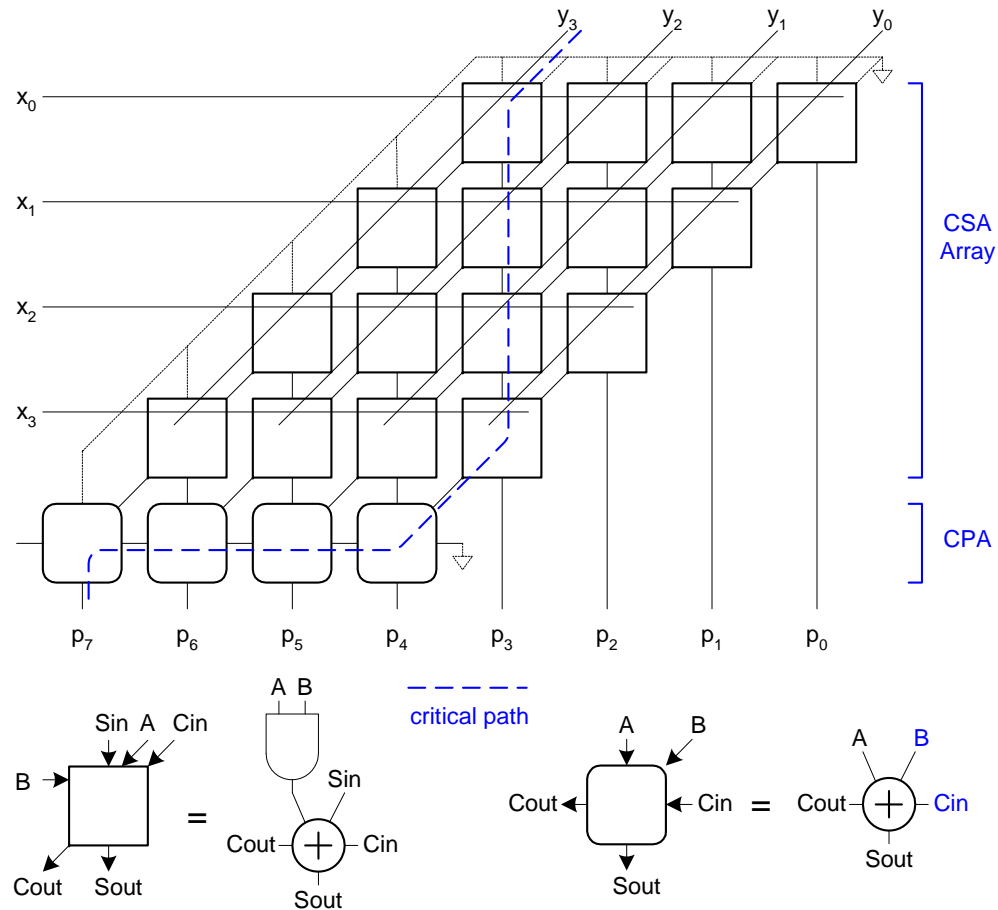

Rectangular Array

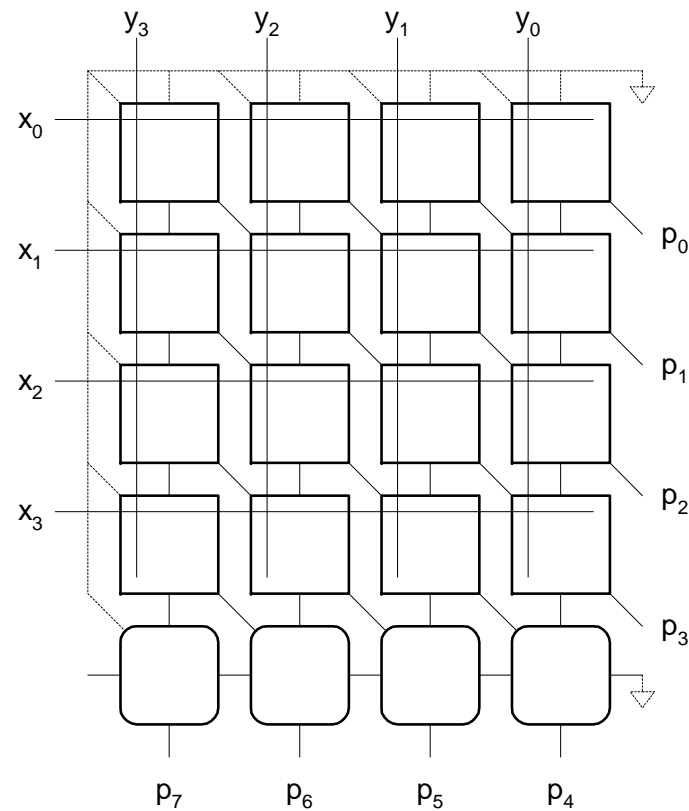- ❑ Squash array to fit rectangular floorplan



Fewer Partial Products

- ❑ Array multiplier requires N partial products
- ❑ If we looked at groups of r bits, we could form N/r partial products.
 - Faster and smaller?
 - Called radix- 2^r encoding
- ❑ Ex: $r = 2$: look at pairs of bits
 - Form partial products of $0, Y, 2Y, 3Y$
 - First three are easy, but $3Y$ requires adder ☹

Booth Encoding

- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | | | |
| 0 | 0 | 1 | Y | | | |
| 0 | 1 | 0 | | | | |
| 0 | 1 | 1 | | | | |
| 1 | 0 | 0 | | | | |
| 1 | 0 | 1 | | | | |
| 1 | 1 | 0 | | | | |
| 1 | 1 | 1 | | | | |

Booth Encoding

- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | | | |
| 0 | 0 | 1 | Y | | | |
| 0 | 1 | 0 | Y | | | |
| 0 | 1 | 1 | | | | |
| 1 | 0 | 0 | | | | |
| 1 | 0 | 1 | | | | |
| 1 | 1 | 0 | | | | |
| 1 | 1 | 1 | | | | |

Booth Encoding

- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | | | |
| 0 | 0 | 1 | Y | | | |
| 0 | 1 | 0 | Y | | | |
| 0 | 1 | 1 | $2Y$ | | | |
| 1 | 0 | 0 | | | | |
| 1 | 0 | 1 | | | | |
| 1 | 1 | 0 | | | | |
| 1 | 1 | 1 | | | | |

Booth Encoding

- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | | | |
| 0 | 0 | 1 | Y | | | |
| 0 | 1 | 0 | Y | | | |
| 0 | 1 | 1 | $2Y$ | | | |
| 1 | 0 | 0 | $-2Y$ | | | |
| 1 | 0 | 1 | | | | |
| 1 | 1 | 0 | | | | |
| 1 | 1 | 1 | | | | |

Booth Encoding

- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | | | |
| 0 | 0 | 1 | Y | | | |
| 0 | 1 | 0 | Y | | | |
| 0 | 1 | 1 | $2Y$ | | | |
| 1 | 0 | 0 | $-2Y$ | | | |
| 1 | 0 | 1 | $-Y$ | | | |
| 1 | 1 | 0 | | | | |
| 1 | 1 | 1 | | | | |

Booth Encoding

- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | | | |
| 0 | 0 | 1 | Y | | | |
| 0 | 1 | 0 | Y | | | |
| 0 | 1 | 1 | $2Y$ | | | |
| 1 | 0 | 0 | $-2Y$ | | | |
| 1 | 0 | 1 | $-Y$ | | | |
| 1 | 1 | 0 | $-Y$ | | | |
| 1 | 1 | 1 | | | | |

Booth Encoding

- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | | | |
| 0 | 0 | 1 | Y | | | |
| 0 | 1 | 0 | Y | | | |
| 0 | 1 | 1 | $2Y$ | | | |
| 1 | 0 | 0 | $-2Y$ | | | |
| 1 | 0 | 1 | $-Y$ | | | |
| 1 | 1 | 0 | $-Y$ | | | |
| 1 | 1 | 1 | $-0 (= 0)$ | | | |

Booth Encoding


- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | Y | 1 | 0 | 0 |
| 0 | 1 | 0 | Y | 1 | 0 | 0 |
| 0 | 1 | 1 | $2Y$ | 0 | 1 | 0 |
| 1 | 0 | 0 | $-2Y$ | 0 | 1 | 1 |
| 1 | 0 | 1 | $-Y$ | 1 | 0 | 1 |
| 1 | 1 | 0 | $-Y$ | 1 | 0 | 1 |
| 1 | 1 | 1 | $-0 (= 0)$ | 0 | 0 | 1 |


Booth Hardware

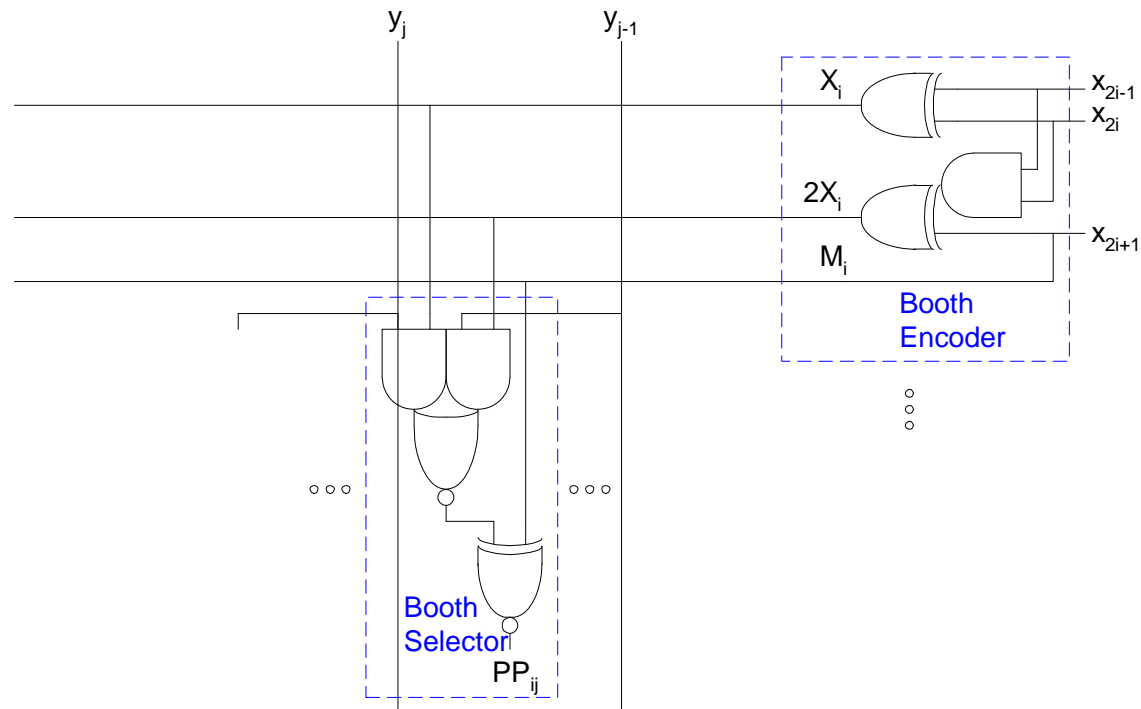- Booth encoder generates control lines for each PP
 - Booth selectors choose PP bits




Sign Extension

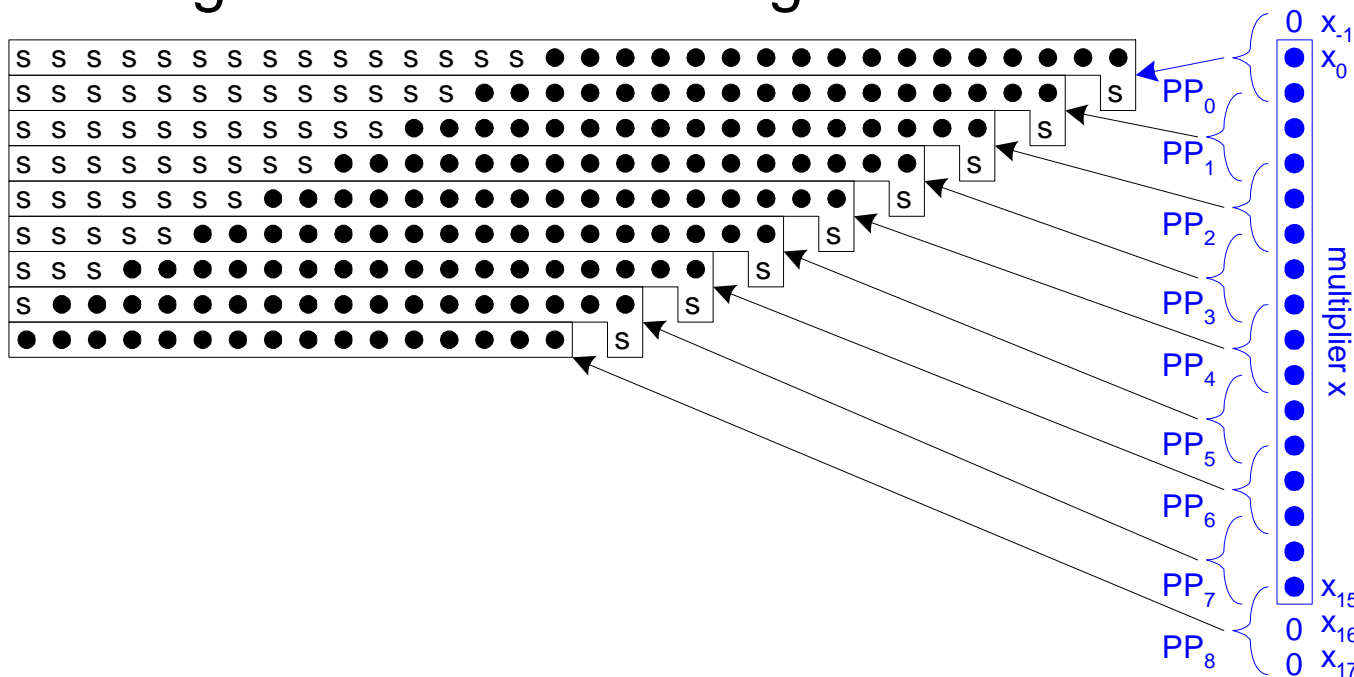- Partial products can be negative
 - Require sign extension, which is cumbersome
 - High fanout on most significant bit




Simplified Sign Ext.

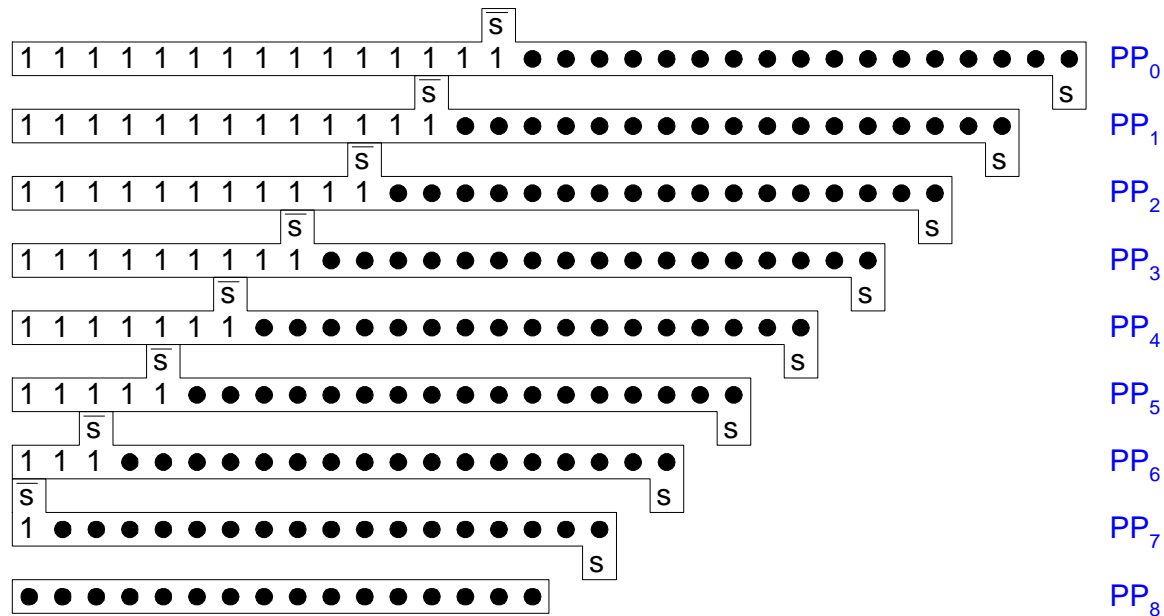- Sign bits are either all 0's or all 1's
 - Note that all 0's is all 1's + 1 in proper column
 - Use this to reduce loading on MSB



Even Simpler Sign Ext.

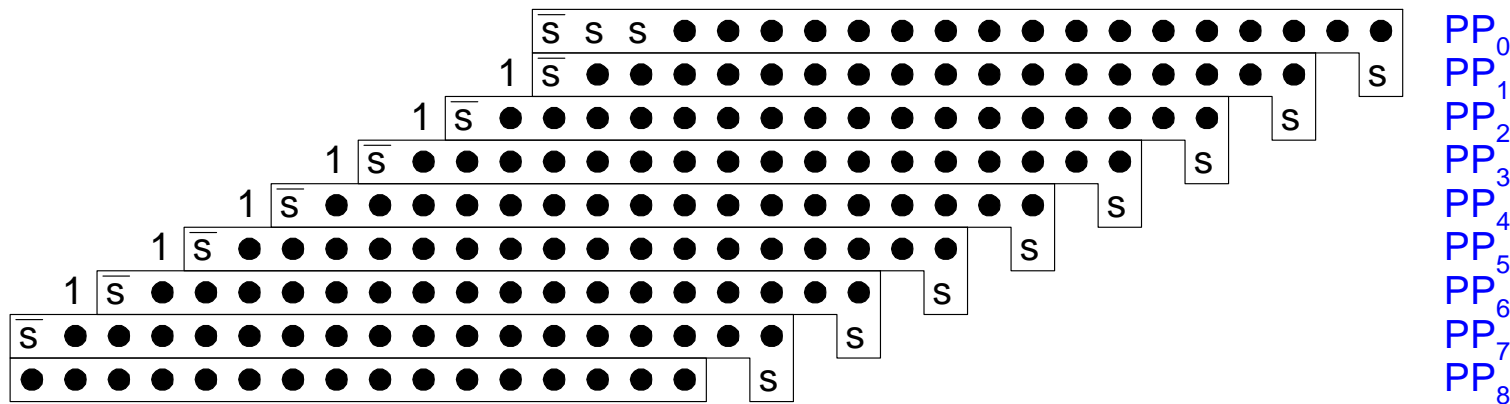- ❑ No need to add all the 1's in hardware
 - Precompute the answer!



Advanced Multiplication

- ❑ Signed vs. unsigned inputs
- ❑ Higher radix Booth encoding
- ❑ Array vs. tree CSA networks